



# ***North South University***

## ***Department of Electrical & Computer Engineering***

### **Lab Report**

<b>Experiment No:</b>	02
<b>Experiment Title:</b>	Design a 4-bit by 4-bit Binary Multiplication Unit.
<b>Course Code:</b>	CSE332L
<b>Course Name:</b>	Computer Organization & Architecture Lab
<b>Name &amp; ID:</b>	Mosroor Mofiz Arman, 1921079642
<b>Date of Experiment:</b>	10.11.2021
<b>Date of Submission:</b>	10.11.2021

## Objectives:

- (i) We have to understand behavior of combinational multiplier from module.
- (ii) We have to understand the theory and implement the multiplication unit.
- (iii) We have to check multiplying bits and show the sum output.

## Equipment list:

- (i) 4 x 7408 AND IC
- (ii) 3 x 7483 or 74283 4bit Adder IC.
- (iii) Trainer Board
- (iv) Wires.

## Block Diagram:

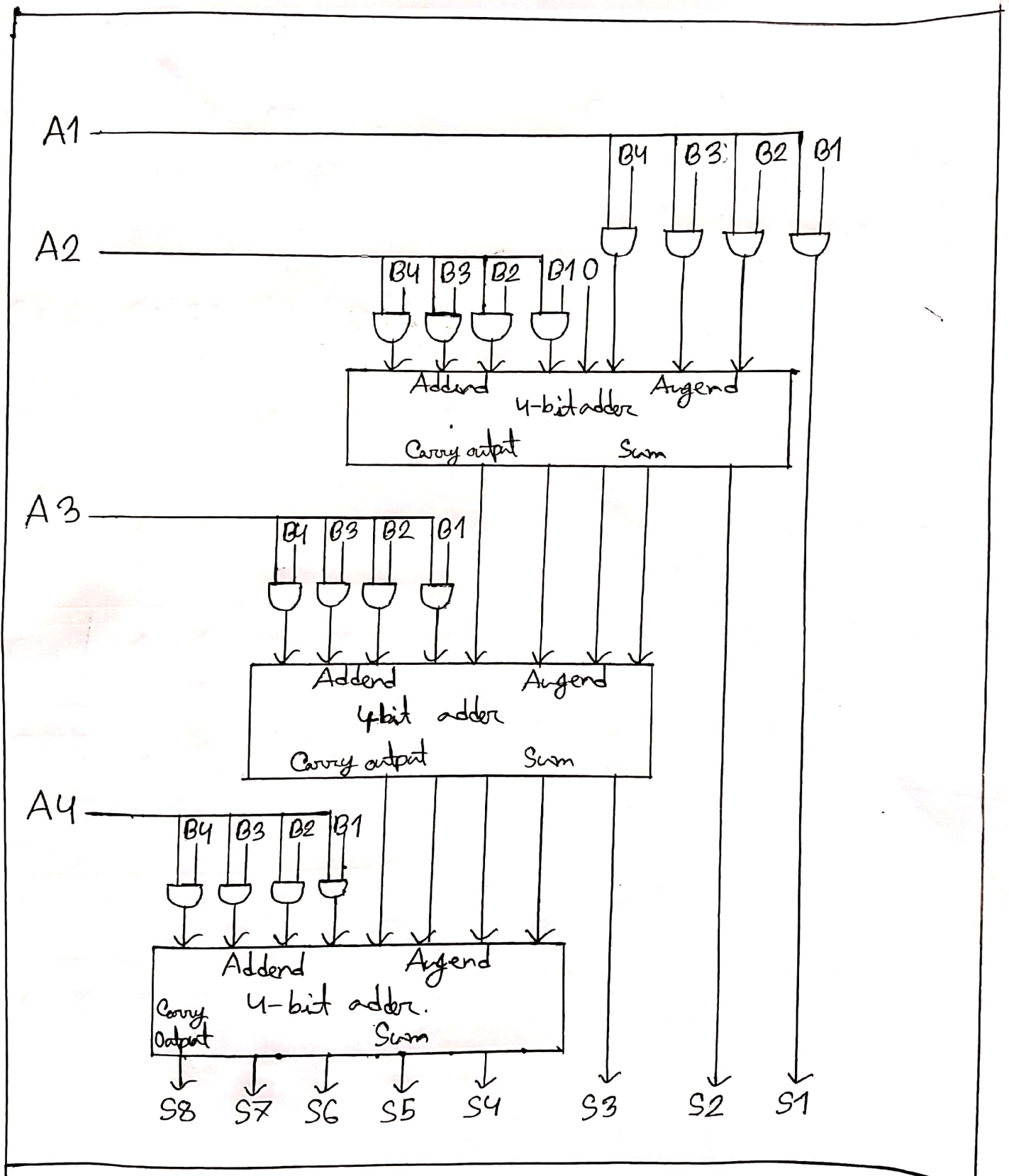



Figure: Block diagram of a 4-bit by 4-bit Binary Multiplier

Table : 2 : Experimental


Multiplicand				Multiplier				Product								Result in Decimal
B <sub>4</sub>	B <sub>3</sub>	B <sub>2</sub>	B <sub>1</sub>	A <sub>4</sub>	A <sub>3</sub>	A <sub>2</sub>	A <sub>1</sub>	S <sub>8</sub>	S <sub>7</sub>	S <sub>6</sub>	S <sub>5</sub>	S <sub>4</sub>	S <sub>3</sub>	S <sub>2</sub>	S <sub>0</sub>	
1	0	0	0	1	0	0	1	0	1	0	0	1	0	0	0	8 × 9 = 72
0	0	0	1	0	0	1	0	0	0	0	0	0	0	1	0	1 × 2 = 2
0	0	1	1	0	1	1	1	0	0	0	1	0	1	0	1	3 × 7 = 21
0	1	0	0	1	0	0	0	0	0	1	0	0	0	0	0	4 × 8 = 32
0	1	0	1	0	1	1	0	0	0	0	1	1	1	1	0	5 × 6 = 30
1	0	0	1	0	1	0	0	0	0	1	0	0	1	0	0	9 × 4 = 36
1	1	1	1	1	0	1	1	1	0	1	0	0	1	0	1	15 × 11 = 165



Pin	
Facing	East
Output?	No
Data Bits	4
Three-state?	No
Pull Behavior	Unchanged
Label	
Label Locat...	West
Label Font	SansSerif ...

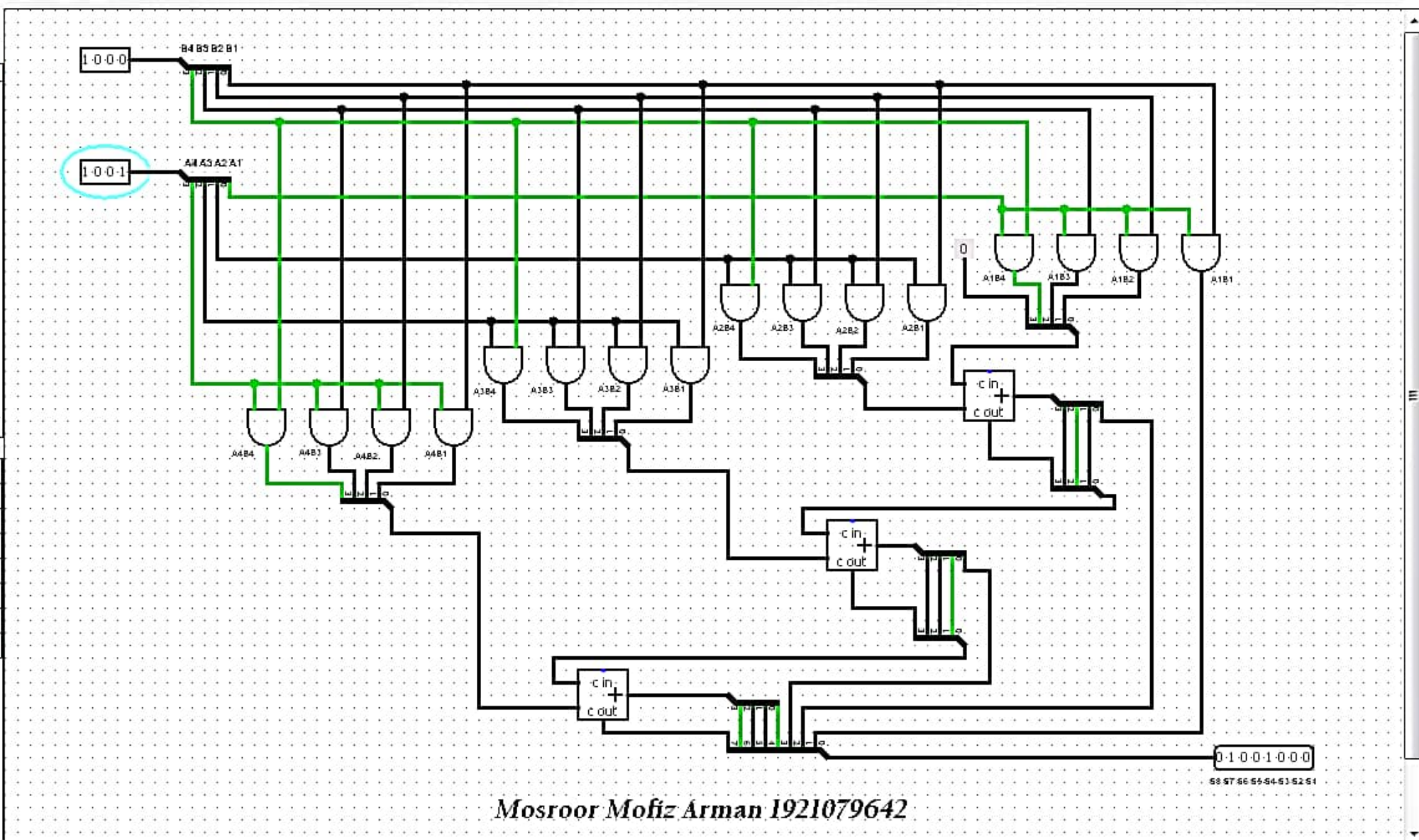


Pin	
Facing	East
Output?	No
Data Bits	4
Three-state?	No
Pull Behavior	Unchanged
Label	
Label Locat...	West
Label Font	SansSerif ...

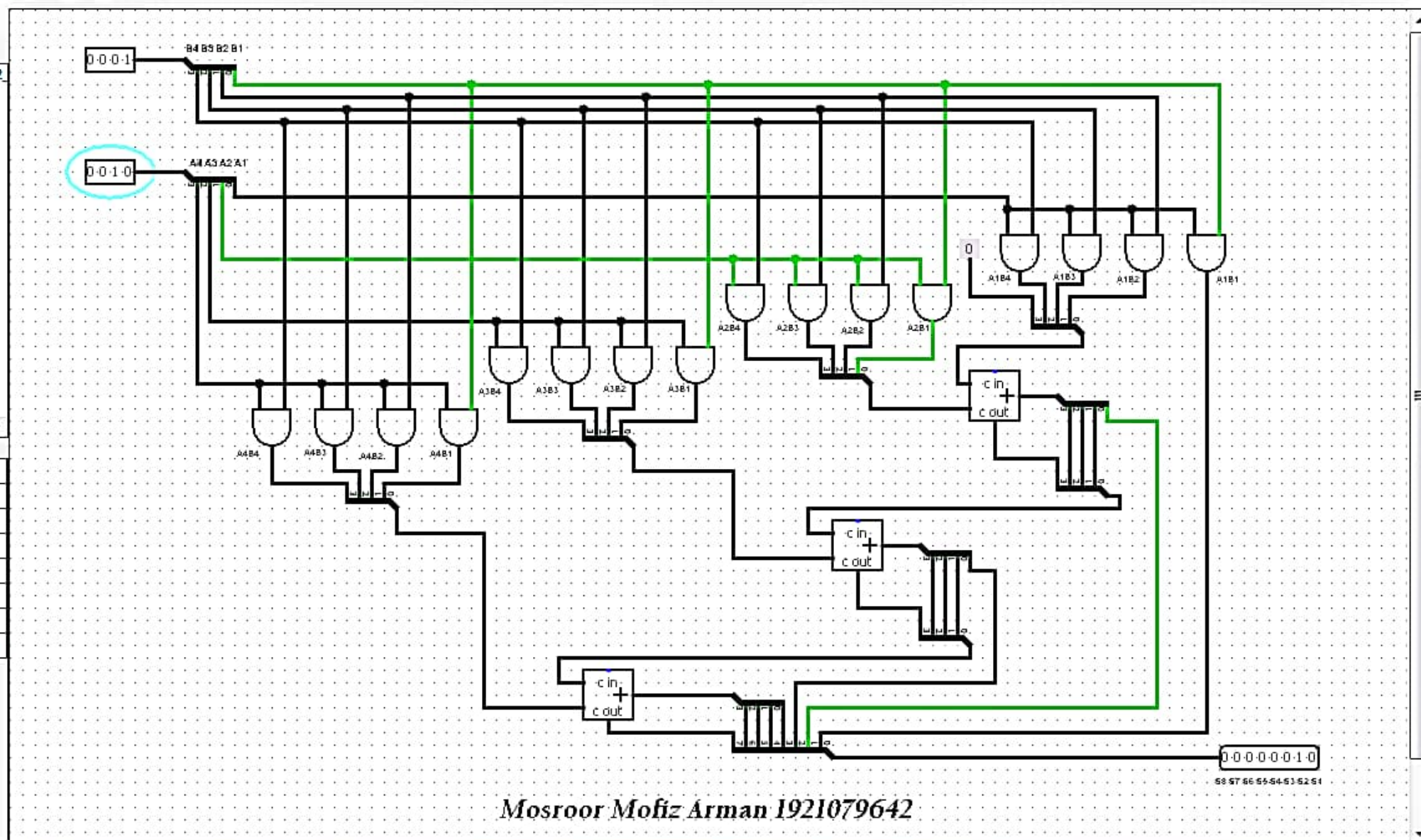

**Mosroor Mofiz Arman 1921079642**



Downloaded from <http://ajph.org/> at University of California, San Diego on November 10, 2014

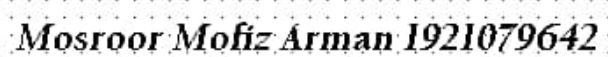


CSE332.6\_1921079642

- main
- Wiring
- Gates
- Plexers
- Arithmetic
- Memory
- Input/Output
- Base

Pin

Facing	East
Output?	No
Data Bits	4
Three-state?	No
Pull Behavior	Unchanged
Label	
Label Locat...	West
Label Font	SansSerif ...

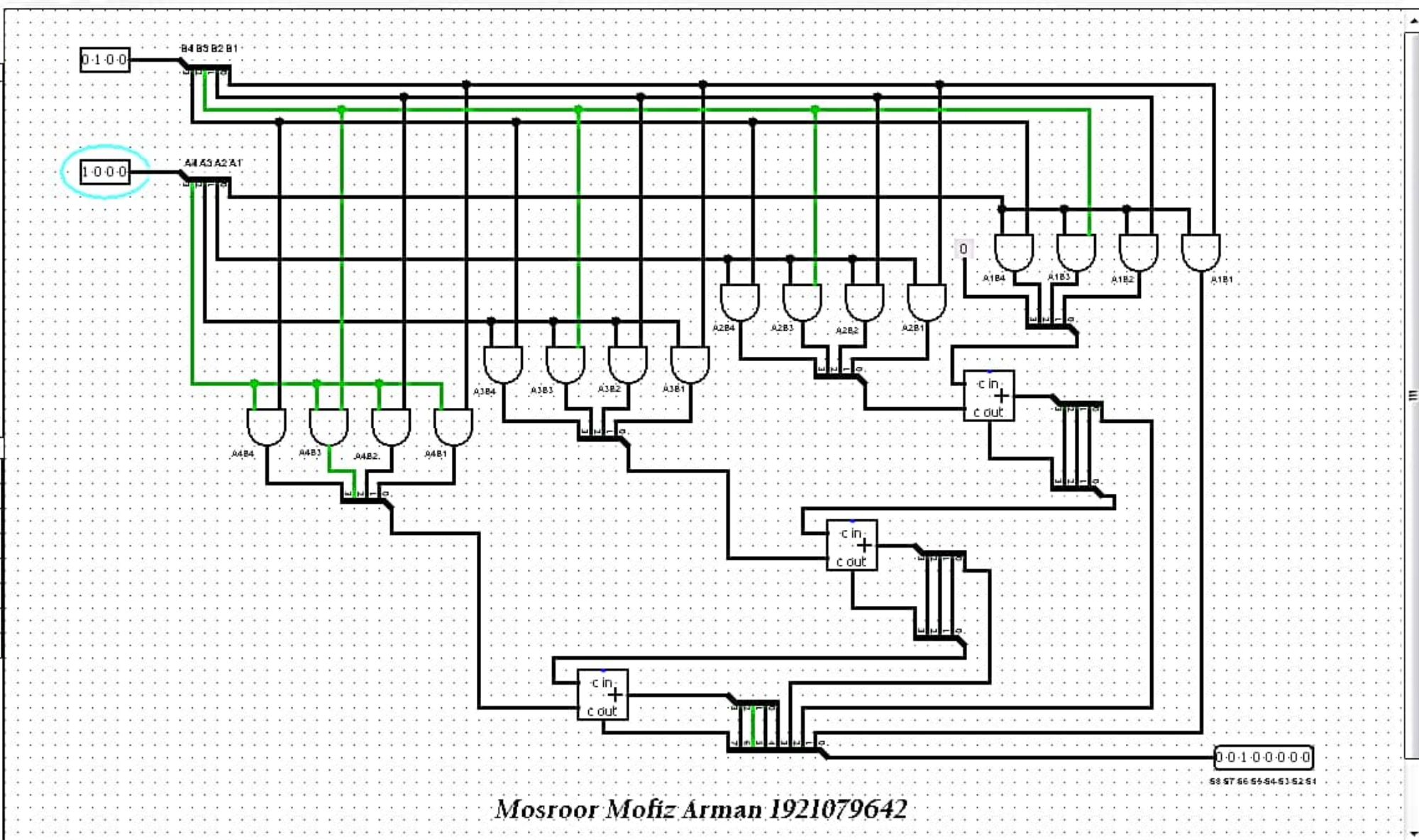


Mosroor Mofiz Arman 1921079642


100%






Pin	
Facing	East
Output?	No
Data Bits	4
Three-state?	No
Pull Behavior	Unchanged
Label	
Label Locat...	West
Label Font	SansSerif ...

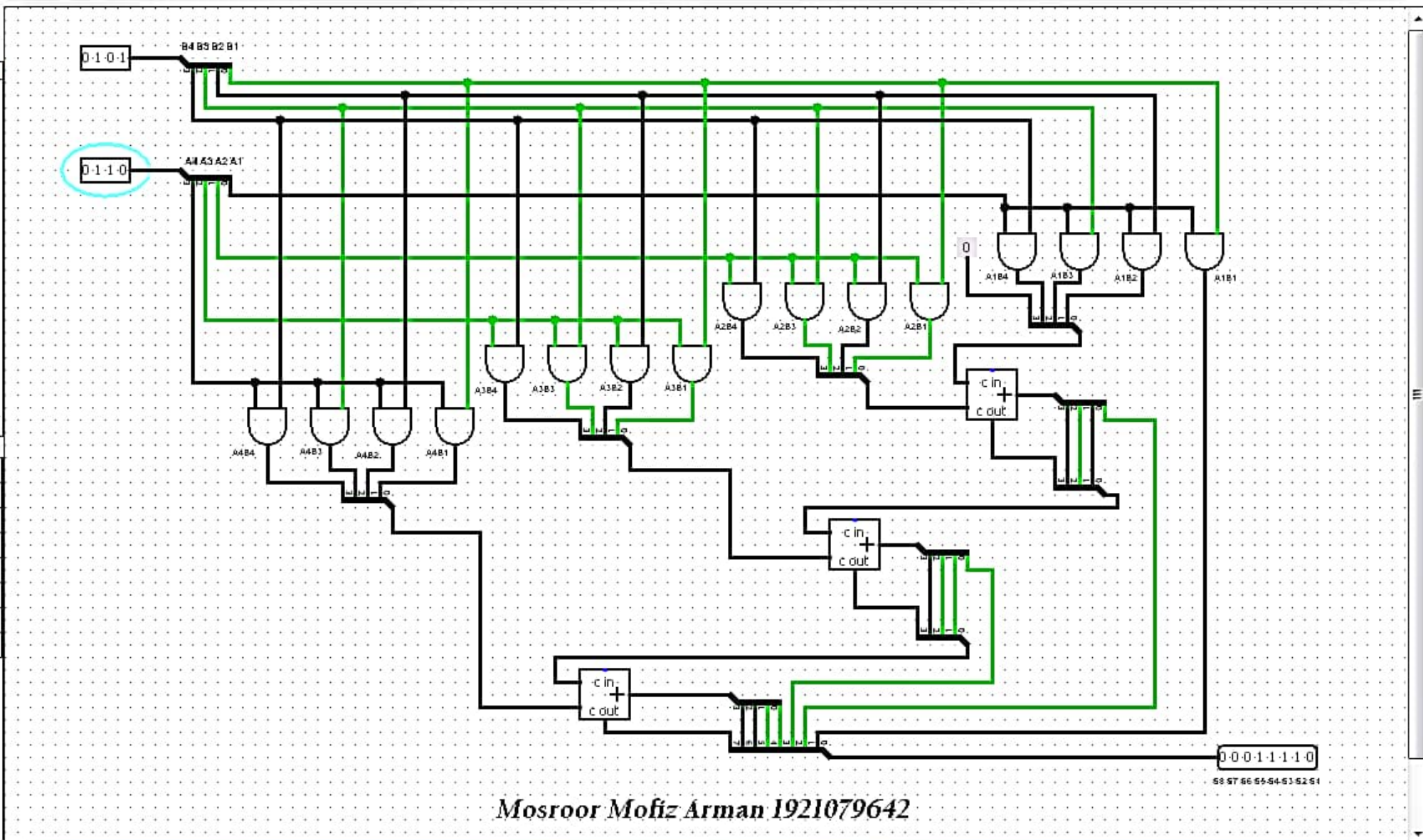

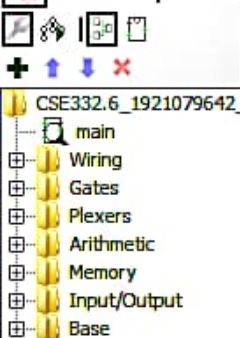


Pin	
Facing	East
Output?	No
Data Bits	4
Three-state?	No
Pull Behavior	Unchanged
Label	
Label Locat...	West
Label Font	SansSerif ...

100%

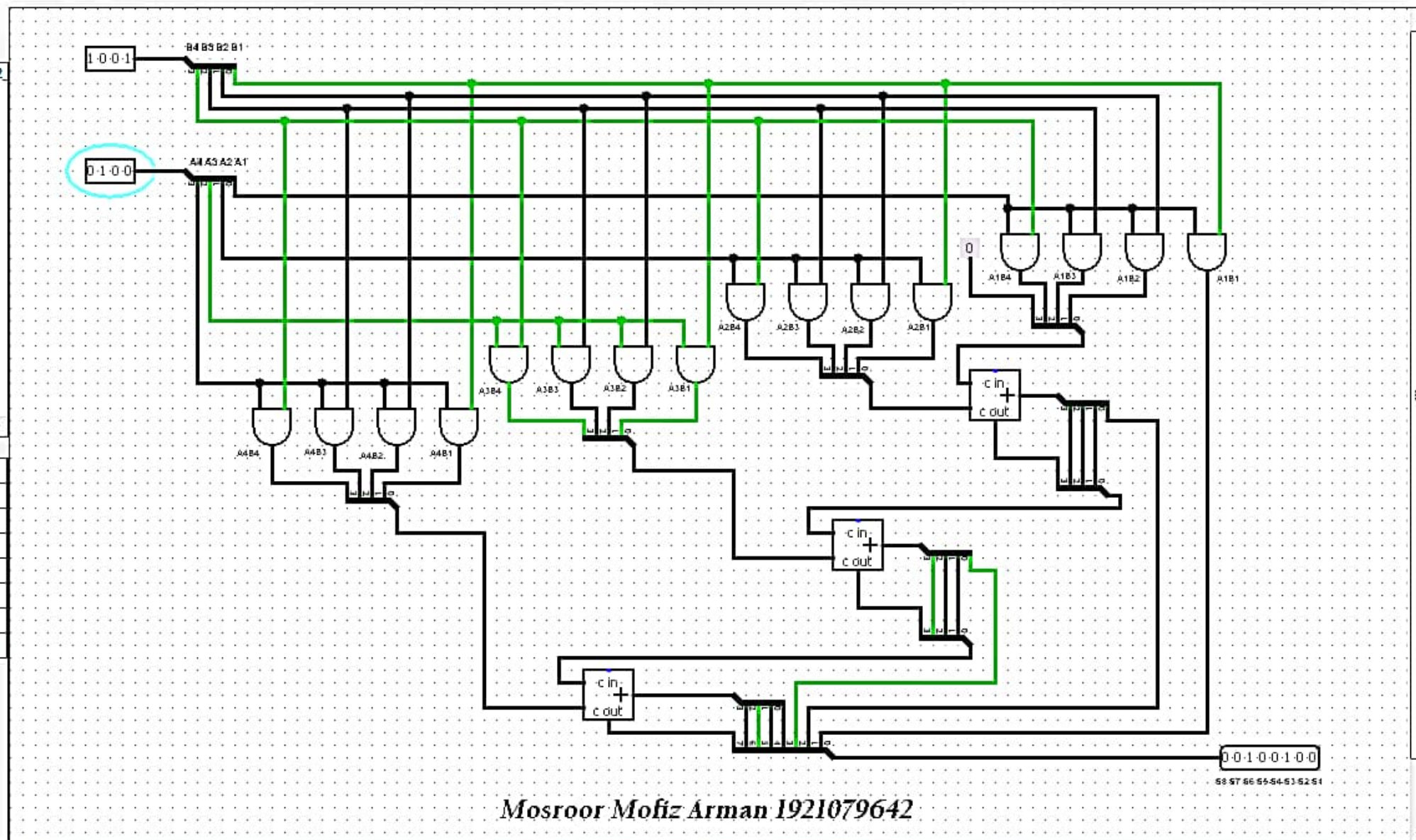



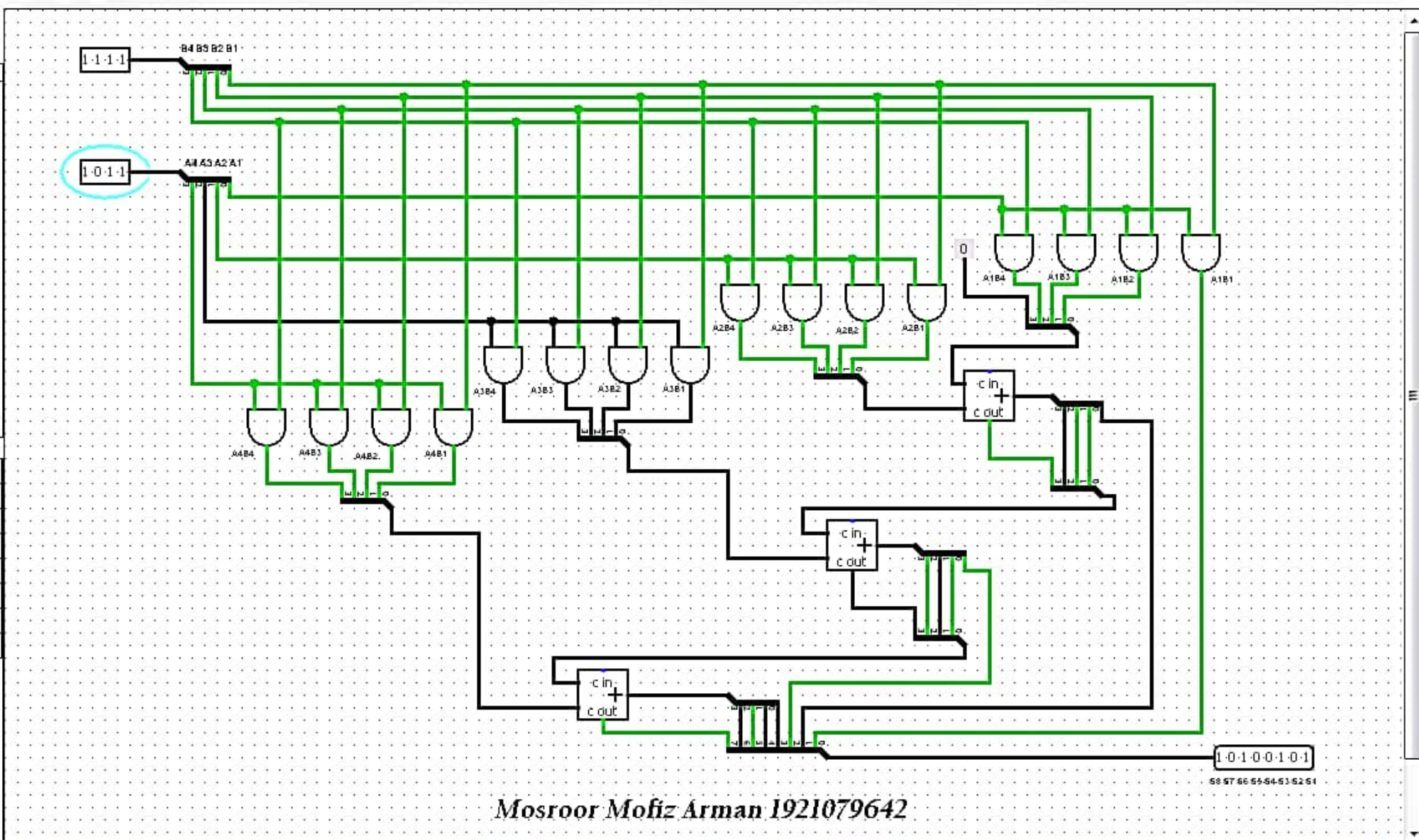

Mosroor Mofiz Arman 1921079642

## Discussion:

In this experiment, we had to design a 4-bit by 4-bit Binary Multiplication Unit with combinational multipliers which do multiplication of two unsigned binary numbers. Each bit of the multiplier is multiplied against the multiplicand, the product is aligned according to the position of the bit with in the multiplier and the resulting products are then summed to form the final result. If the multiplier bit is 1, the product is an appropriately shifted copy of the multiplicand, if the multiplier bit is a 0, the product is simply 0. We had used Logixim software and designed the logic part using Logixim software. That's why we didn't have to deal with any hardware instructions. After designing the logic part, we had to check the multiplying bits and the sum outputs from the Logixim software and submit the (.circ) file to our lab instructor on the Canvas platform.