

North South University

Department of Electrical & Computer Engineering

Lab Report

Experiment No: 03

Experiment Title: Design of a 2-bit Arithmetic Unit.

Course Code: CSE332L

Course Name: Computer Organization & Architecture Lab


Name & ID: Mosroor Mofiz Arman, 1921079642

Date of Experiment: 17.11.2021

Date of Submission: 17.11.2021

Objectives: (i) we have to know about NOT gates. (ii) We have to construct a 2-bit withmetic wind. (iii) he have to know about adder and how to add and subtract two 2-bit inputs using adder. (iv) we have to know about MUX and implementing 4:1 MUX. 0011001001 Add with our Equipment list. (i) Trainer board (ii) IC 7404, 7483, 74F163. (iii) Wires for Connection. PERDIPOR ALAO TOU + 1= Iroum 1101100101 A kuma soll DEMOGRAPH OF PORTA 11/10001011 A squaret 4moil - 1+11+0A1/ Table: 2-bit arithmetic emit south table:

Block Diagram:

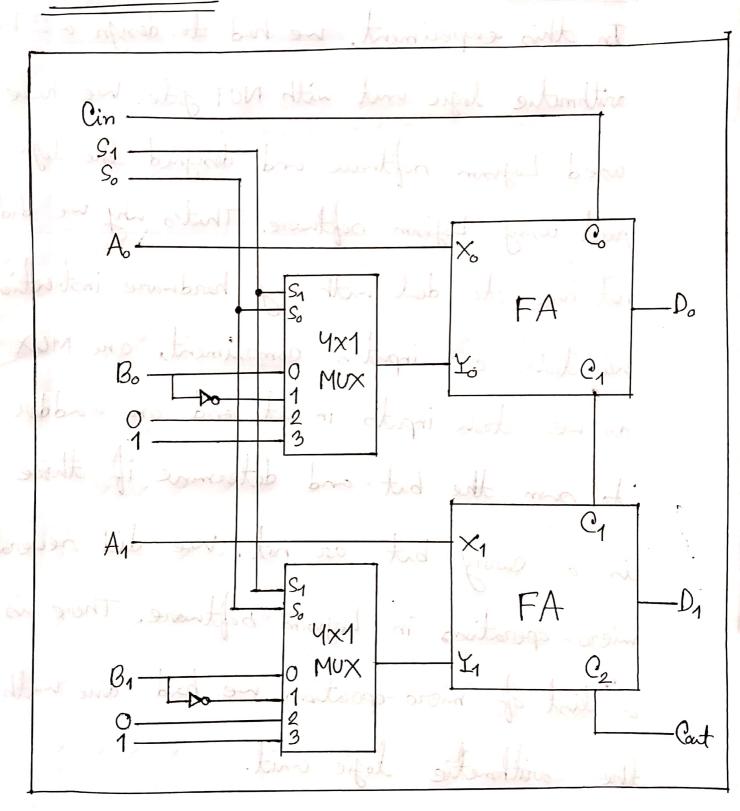


Figure! A 2-bit Arithmetic Unit (Block Diagram)


Truth table

white I'M trade was of your and in												
		البذار	ini	Lx	L			ton	J. Coroll	07	. 3	in and Ob
	S1	SC	Ci	in A	1	AC	131	BO	D1	Do	Cont	Microoperation
Ġ	di	10	brus	C.	Lx	ri	***	2-1	owt		ton	the bos
	0	O	C) ()	0	0	1	0	1	0	Add
\$ t.	0	0	1	,	1	0	0	1	O,	0	1	Add with carry
	0	1	C			1	0	0	0	O	1	Subtract with Bosown
	0	1	1	C)	1	1 .2	1	1	0	0	Subtract.
	1	0	0	>	1	1	0	1	1	1	0	Transfer A A1A0+00+0 = Transfer A
	1	0	1	1		0	1	0	1	1	0	Ironement A A1A0+00+1=IronementA
	1	1	0	1		1	0	0	1	0		Decrement A A1 A0 + 11+0 = Pecrement A
	1	1	1	1	1	0	0	0	1	0	1	Transfer A A1A0 + 11+1 = Transfer A


Table: 2-bit withmetic unit truth table.

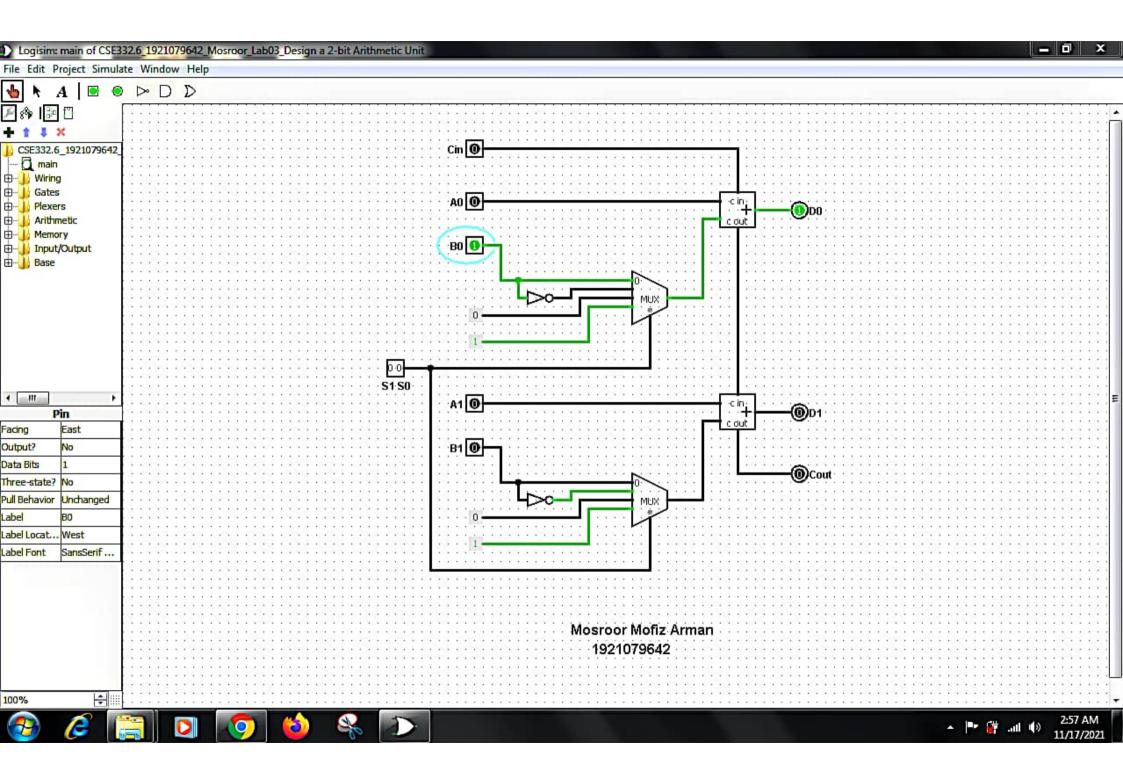


Add

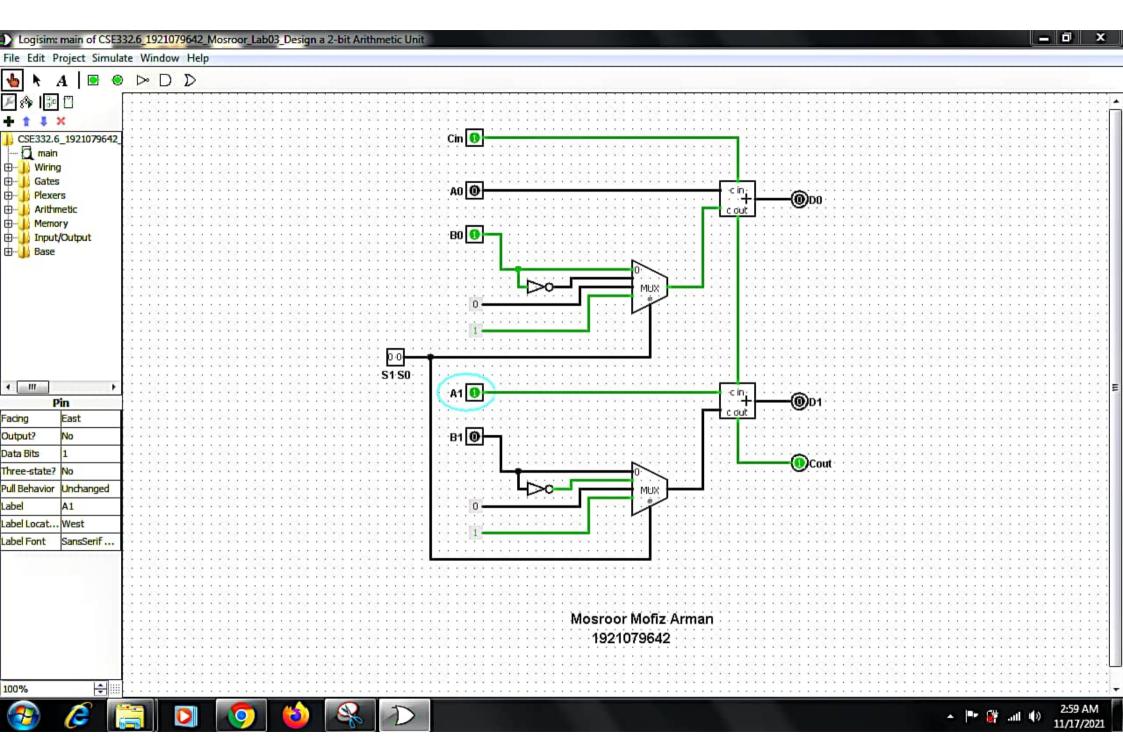


Add with Carry

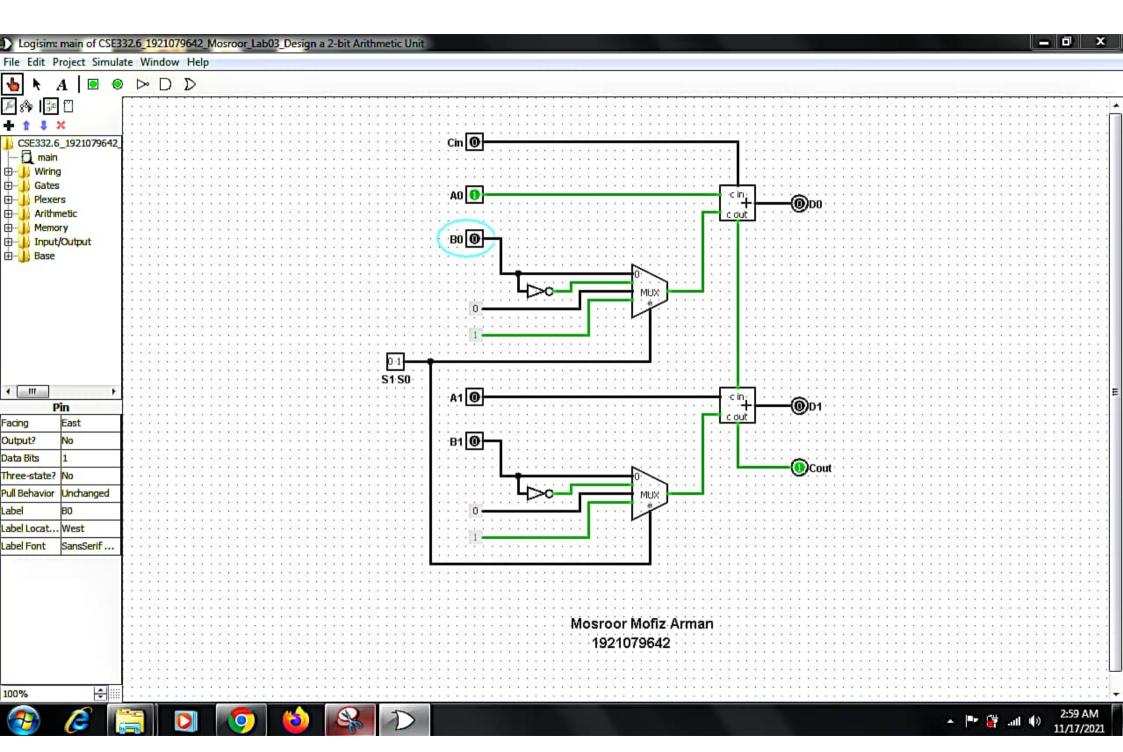


Subtract with Borrow

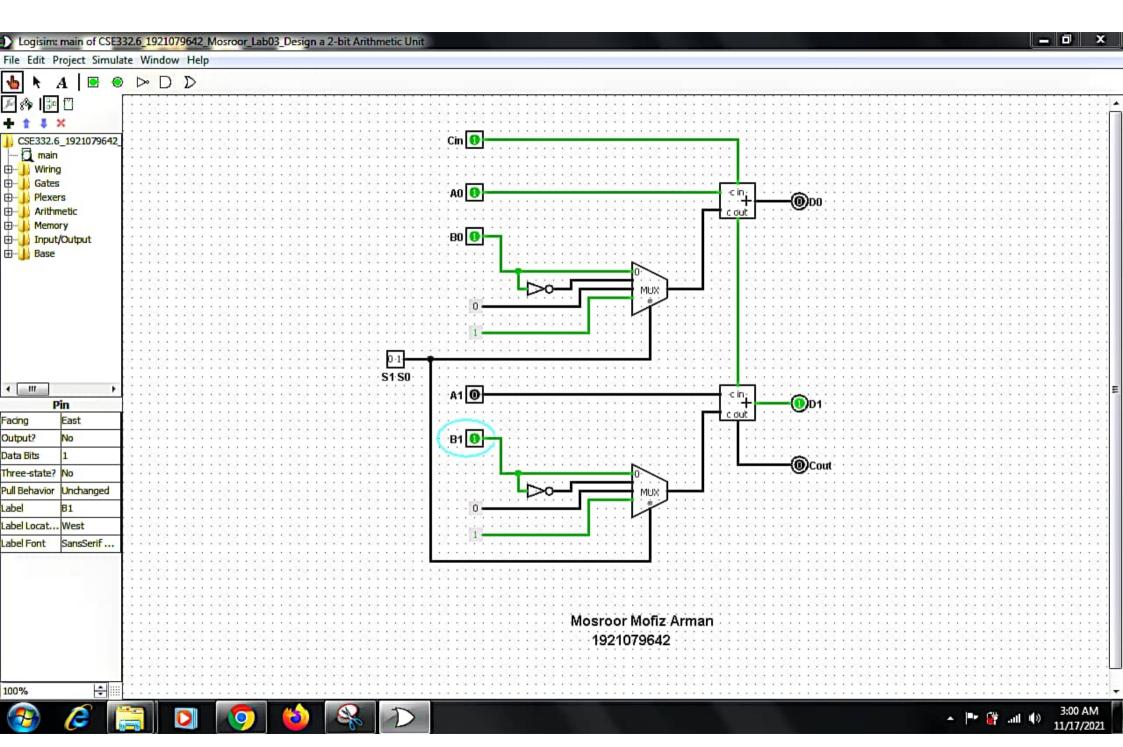


Subtract

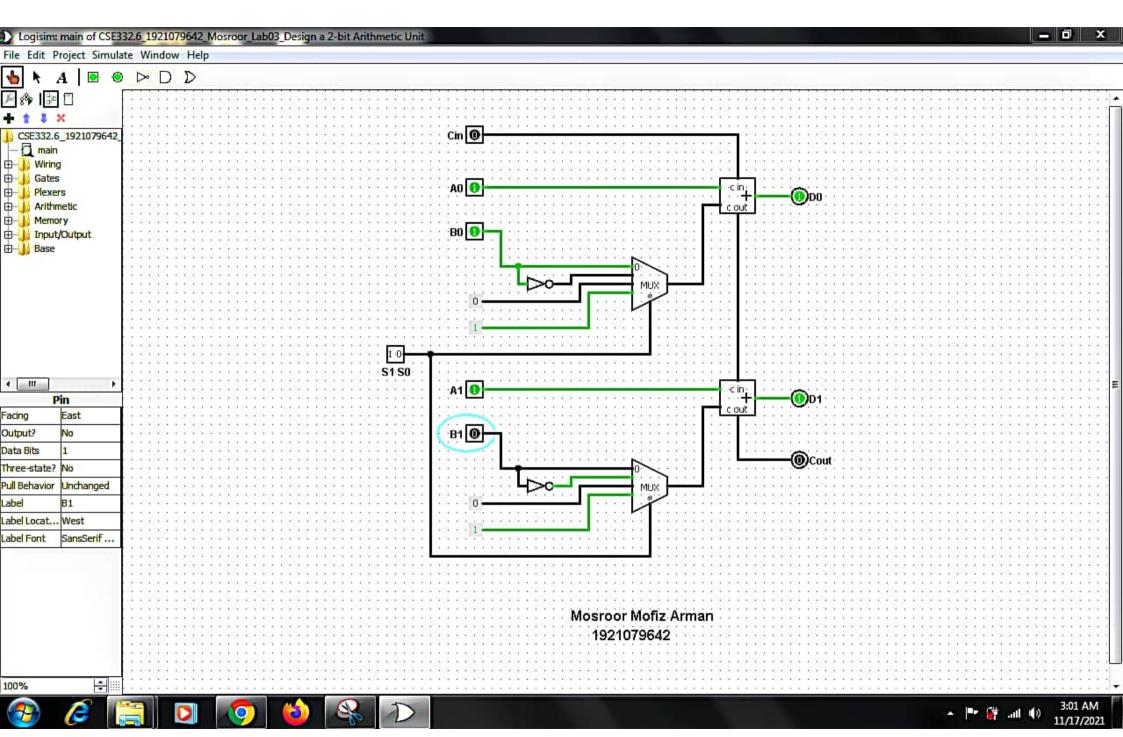


Transfer A(A1 A0 + 0 0 + 0 = Transfer A)

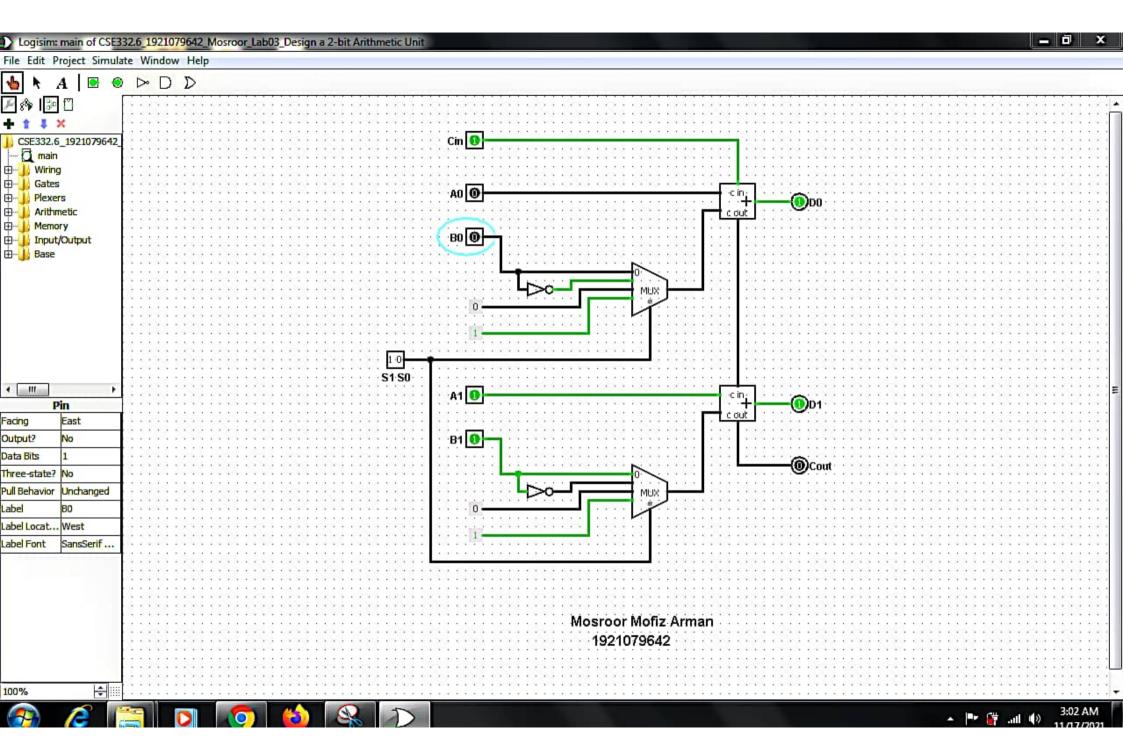

Increment A

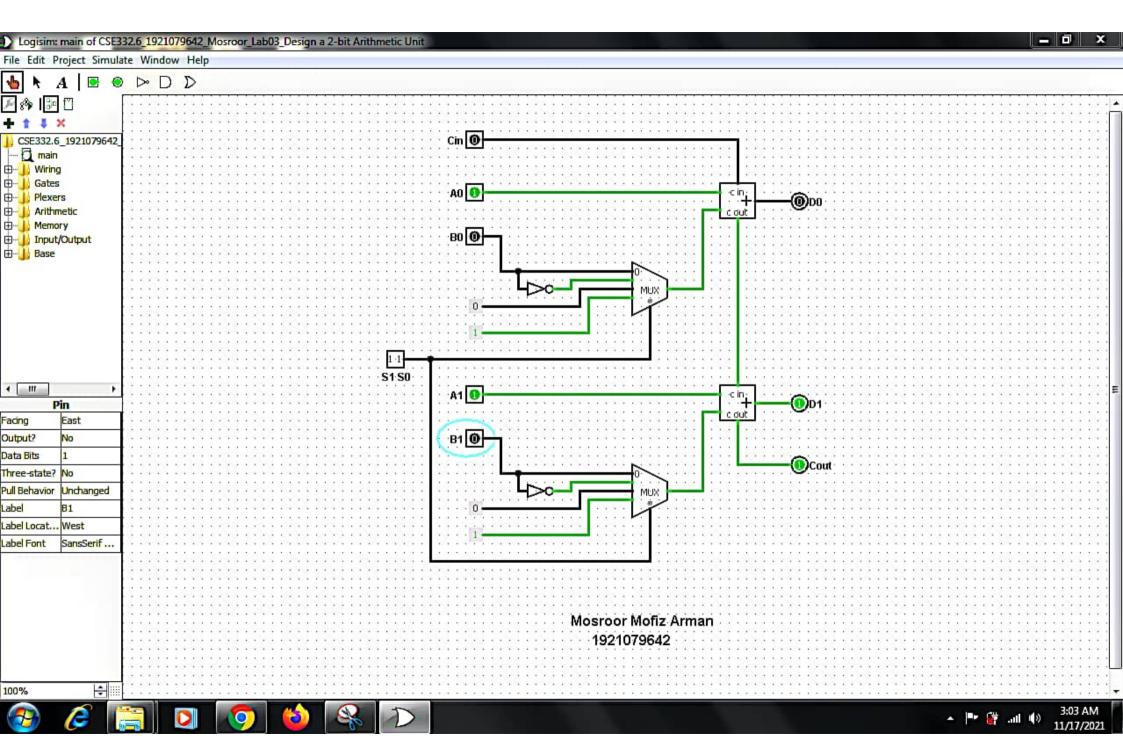

Decrement A

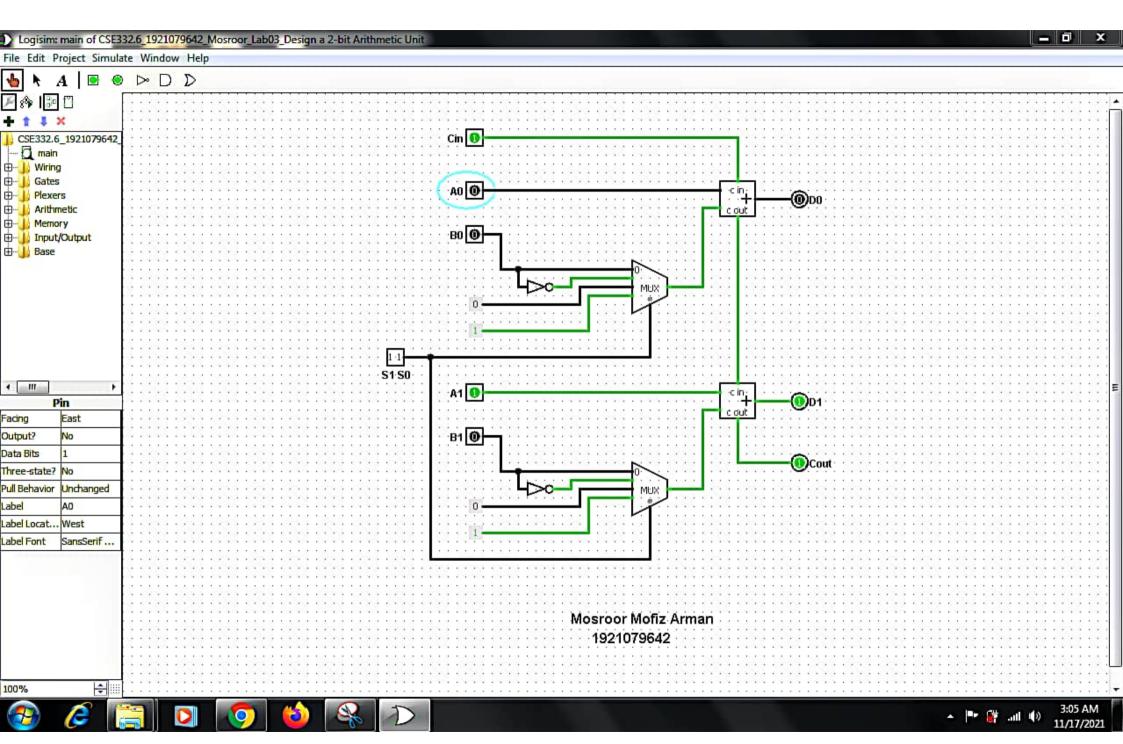

Transfer A(A1 A0 + 1 1 + 1 = Transfer A)

Discussion:

In this experiment, we had to design a 2-bit arithmetic logic anit with NOT gate. We have used Logisim software and designed the logic part using Legisim software. That's why we did not have to deal with any hardware instructions. uce table one inputs compliment, one MUX as we took inputs in it and one adder to am the bit and determine if there is a carry bit on not. we did several micro-operations in Laginim nathware. There is a list of micro-operations we had done with the withmetic logic unit.

Figure A 2 but ibrithmelie Unit (

1. Add.

- (2) Add with earory
- (3) Subtract with bosoow
- (4) Subtract
- (5) Transfer A
- (6) Increment A
- (7) Decrement A
- (8) Transfer A.

After designing the logic part, we had to check the circuit for the above micro-operations and inserted the value of the following micro-operations from the logissim circuit to the truth table. Finally, we had submitted the (circ) finally, we had submitted the (circ) finally, are had submitted the (circ) finally, are had submitted the (circ) finally, are had submitted the (circ)