



North South University

Department of Electrical & Computer Engineering

Lab Report

Experiment No:	01
Experiment Title:	Design of a 2-bit Logic unit.
Course Code:	CSE332L
Course Name:	Computer Organization & Architecture Lab
Name & ID:	Mosroor Mofiz Arman, 1921079642
Date of Experiment:	03.11.2021
Date of Submission:	06.11.2021

Objectives:

(i) we have to construct a 2-bit logic unit that is a part of an ALU and this logic unit will have four micro-operations: AND, OR, XOR and NOT operations.

(ii) Logic micro-operations are very useful for manipulating individual bits or portions of a word stored in a register.

(iii) We can change bit values by this operation, delete a group of bits, or insert a new set of bits in a register.

(iv) We have to design a 2-bit logic unit that will give two outputs:

one output for each of the 2 bits.

Equipment list:

- (i) Trainer board.
- (ii) IC 7404, 7408, 7432, 7486, 74F153.
- (iii) Wires for connection.

Block Diagram:


 


Figure: Block diagram of a 2bit logic unit.

Truth Table :


A1	A0	B1	B0	AND1	AND0	OR1	OR0	XOR1	XOR0	NOT A1	NOT A0
0	0	0	0	0	0	0	0	0	0	1	1
0	0	0	1	0	0	0	1	0	1	1	1
0	0	1	0	0	0	1	0	1	0	1	1
0	0	1	1	0	0	1	1	1	1	1	1
0	1	0	0	0	0	0	1	0	1	1	0
0	1	0	1	0	1	0	1	0	0	1	0
0	1	1	0	0	0	1	1	1	1	1	0
0	1	1	1	0	1	1	1	1	0	1	0
1	0	0	0	0	0	1	0	1	0	0	1
1	0	0	1	0	0	1	1	1	1	0	1
1	0	1	0	1	0	1	0	0	0	0	1
1	0	1	1	1	0	1	1	0	1	0	1
1	1	0	0	0	0	1	1	1	1	0	0
1	1	0	1	0	1	1	1	1	0	0	0
1	1	1	0	1	0	1	1	0	1	0	0
1	1	1	1	1	1	1	1	0	0	0	0

Table : 2-bit logic unit.

 


- CSE332.6_1921079642_Mosroor_Lab01_Design of a 2-bit Logic unit*
 - main
 - Wiring
 - Gates
 - Plexers
 - Arithmetic
 - Memory
 - Input/Output
 - Base

Circuit: main	
Circuit Name	main
Shared Label	
Shared Label Facing	East
Shared Label Font	SansSerif Plain 12

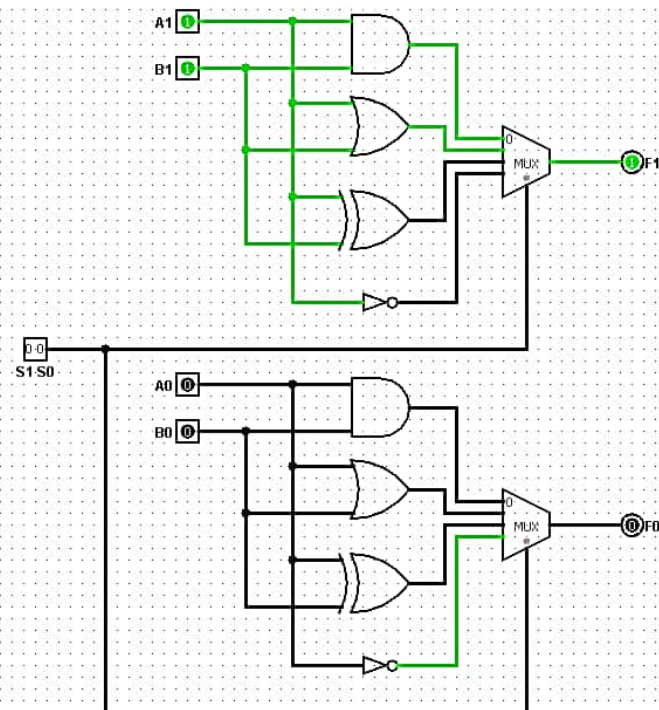


Mosroor Mofiz Arman
1921079642

 


- CSE332.6_1921079642_Mosroor_Lab01_Design of a 2-bit Logic unit*
- main
- Wiring
- Gates
- Plexers
- Arithmetic
- Memory
- Input/Output
- Base

	Pin
Facing	East
Output?	No
Data Bits	1
Three-state?	No
Pull Behavior	Unchanged
Label	B0
Label Location	West
Label Font	SansSerif Bold 12

 


Mosroor Mofiz Arman
1921079642

 

- CSE332.6_1921079642_Mosroor_Lab01_Design of a 2-bit Logic unit*
 - main
 - Wiring
 - Gates
 - Plexers
 - Arithmetic
 - Memory
 - Input/Output
 - Base

	Pin
Facing	East
Output?	No
Data Bits	1
Three-state?	No
Pull Behavior	Unchanged
Label	A0
Label Location	West
Label Font	SansSerif Bold 12

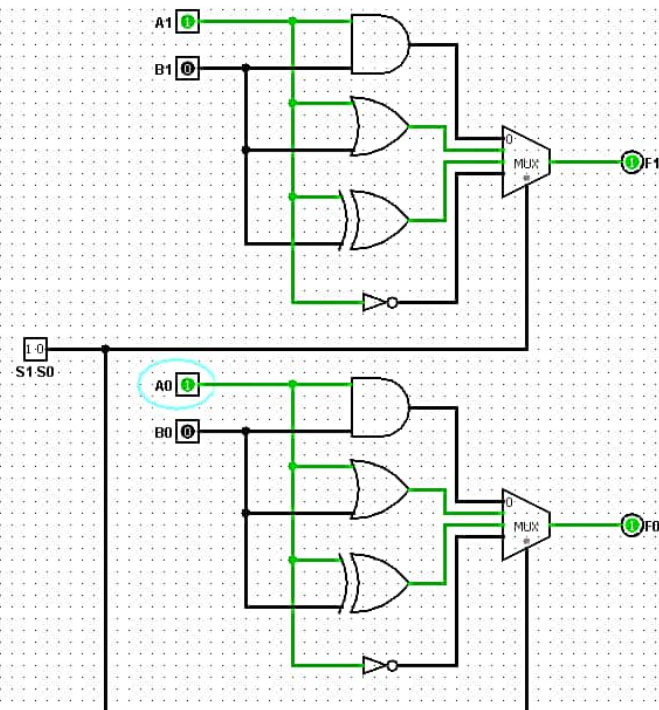


Mosroor Mofiz Arman
1921079642



- CSE332.6_1921079642_Mosroor_Lab01_Design of a 2-bit Logic unit*
- main
- Wiring
- Gates
- Plexers
- Arithmetic
- Memory
- Input/Output
- Base

	Pin
Facing	East
Output?	No
Data Bits	1
Three-state?	No
Pull Behavior	Unchanged
Label	B1
Label Location	West
Label Font	SansSerif Bold 12

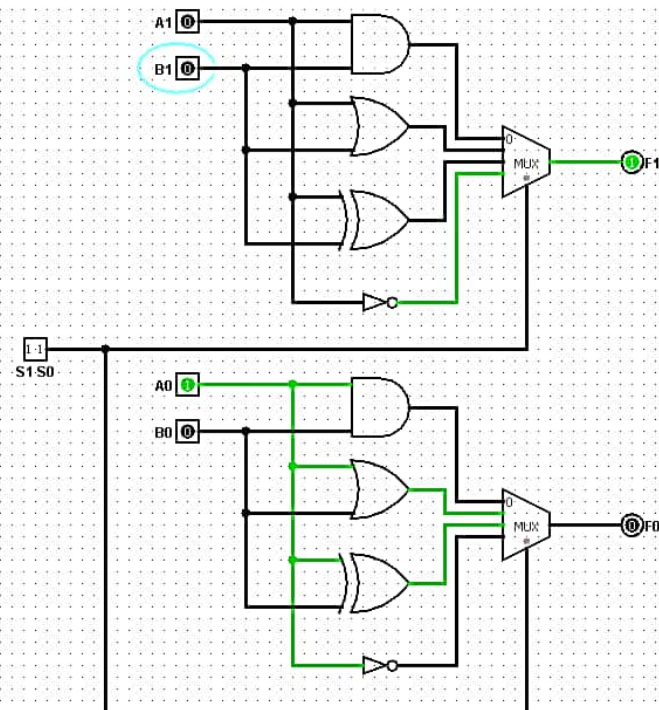

Mosroor Mofiz Arman
1921079642



Discussion :

In this experiment, we had to design a 2bit logic unit with AND, OR, XOR and NOT gate with two different 4×1 MUX. We have used Logisim software and designed the logic part using Logisim software; that's why we didn't have to deal with any hardware instructions. We took two inputs for every MUX, which were A_0, B_0 for the MUX and A_1, B_1 for the second MUX. The selection bits of the MUX were used to choose the gates. The selection sequence, which was the same for both MUX, was given below:

Selection Bit		Gates
S_1	S_0	
0	0	AND Gate
0	1	OR Gate
1	0	XOR Gate
1	1	NOT Gate